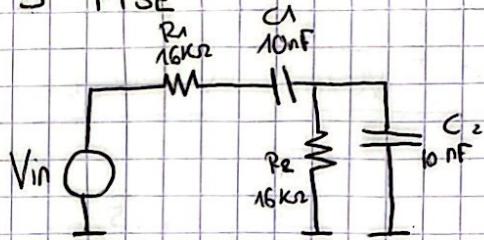


Estudi previ practica 5 FISE

Qüestió EP1



Analisi del filtre passabanda passiu RC

Qüestió EP1

$$V_{out} = \frac{Z_2}{Z_1 + Z_2} V_{in}$$

~~z1 = R + 1/Cs~~

$$Z_1 = R + \frac{1}{Cs} = \boxed{\frac{R(s+1)}{Rs}}$$

$$Z_2 = R // \frac{1}{Cs} = \frac{R^{-1}/Cs}{R + 1/Cs} = \boxed{\frac{R}{R(s+1)}}$$

$$H(s) = \frac{V_o}{V_i} = \frac{Z_2}{Z_1 + Z_2} = \frac{\frac{R}{R(s+1)}}{\frac{R(s+1)^2 + Rs}{Cs(Rs)}} = \frac{R}{Rs+1} \frac{Cs(Rs+1)}{R(s+1)^2 + Rs} =$$

$$= \frac{Rcs}{R^2 C^2 s^2 + 2Rcs + 1 + Rcs} = \frac{Rcs}{R^2 C^2 s^2 + 3Rcs + 1} = \frac{Rcs}{R^2 C^2 (s^2 + \frac{3s}{RC} + \frac{1}{R^2 C^2})} =$$

$$\boxed{\frac{s/RC}{s^2 + \frac{3s}{RC} + \frac{1}{R^2 C^2}}}$$



Qüestió EP2

$$\boxed{\omega_0 = \frac{1}{RC}}$$

$$\boxed{A = 1}$$

$$\frac{3}{RC} = \frac{1}{RC} \cdot \frac{1}{Q} \rightarrow$$

$$\boxed{Q = \frac{1}{3}}$$



Qüestió EP3

$$S = \frac{-\frac{3}{RC} \pm \sqrt{(\frac{3}{RC})^2 - U \cdot (\frac{1}{RC})^2}}{2} = \frac{-\frac{3}{RC} \pm \sqrt{5} (\frac{1}{RC})^2}{2} =$$

$$= \frac{-\frac{3}{RC} + \frac{\sqrt{5}}{RC}}{2} = \frac{-3 + \sqrt{5}}{2RC}$$


$$= \frac{-\frac{3}{RC} - \frac{\sqrt{5}}{RC}}{2} = \frac{-3 - \sqrt{5}}{2RC}$$



$$|H(j\omega_0)| = \frac{\omega \cdot \omega_0}{\sqrt{\omega^2 + (0,38 \cdot \omega_0)^2} \cdot \sqrt{\omega^2 + (2,62 \cdot \omega_0)^2}} =$$

$$= \frac{\omega_0^2}{\omega_0 \sqrt{1 + (0,38)^2} \cdot \omega_0 \sqrt{1 + (2,62)^2}} =$$
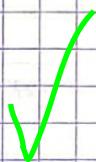
$$= \frac{1}{\sqrt{9}} = \boxed{\frac{1}{3}}$$




Qüestió EP4

$$\omega_0 = \frac{\lambda}{RC} = \frac{1}{16 \cdot 10^3 \cdot 10 \cdot 10^{-9}} = \boxed{6250 \text{ rad/s}}$$

$$\hookrightarrow f_0 = \frac{\omega_0}{2\pi} = \frac{6250}{2\pi} = \boxed{994,72 \text{ Hz}}$$
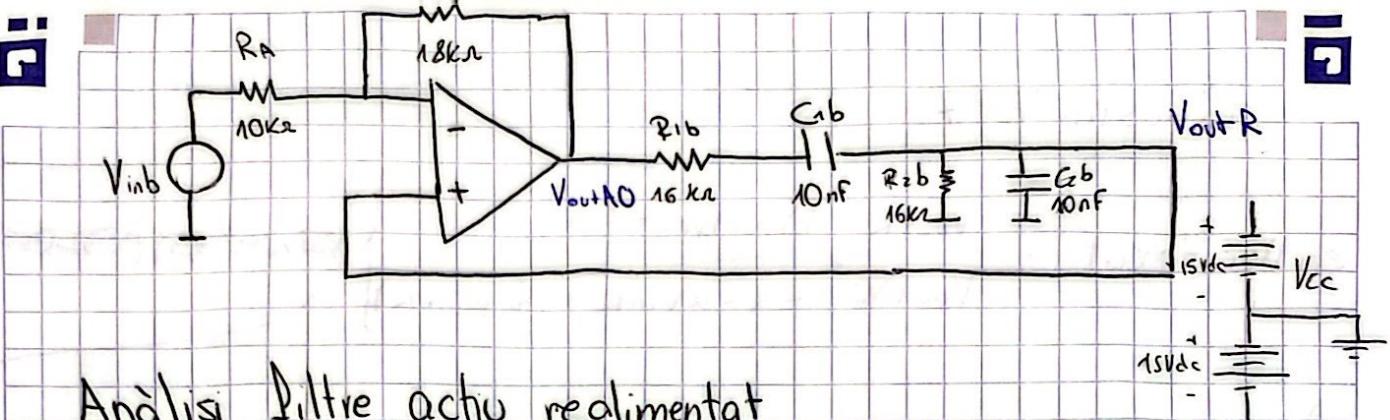
$$A \in \omega_0 \not= 6250 \not= \rightarrow \boxed{A = 1}$$





Anàlisi filtre actiu realimentat

Qüestió EP5 · Al considerar l'AO ideal, reavars

$$V_{outR} = 0 \quad \text{pota positiva AO}$$

$V_{inR} = 0$ CCV

$$V_{outAO} = \frac{-R_F}{R_A} \cdot V_{inR}$$

$$\frac{V_{outR} - V_{outAO}}{R_A} = \frac{V_{outR} - V_{outAO}}{R_F}$$

$$\frac{V_{outAO}}{V_{inR}} = \left[\frac{-R_F}{R_A} = \alpha \right]$$

$$\frac{V_{outAO}}{R_F} = \frac{V_{outR}}{R_A} \rightarrow \frac{V_{outR}}{R_F}$$

$\alpha = \frac{-R_F}{R_A}$

$$\frac{V_{outAO}}{R_F} = V_{outR} \left(\frac{1}{R_A} + \frac{1}{R_F} \right)$$

$$\frac{V_{outAO}}{V_{outR}} = \left(1 + \frac{R_F}{R_A} \right) = -f_R$$

$-f_R = 1 + \frac{R_F}{R_A}$

Qüestió EP6

$$T(s) = H(s) \cdot f_R =$$

$$= \frac{1/R_C \cdot s}{s^2 + s^3/R_C + (1/R_C)^2} \left(-1 \right) \left(\frac{R_F}{R_A} + 1 \right) =$$

$= \frac{-\frac{s}{R_C} \left(1 + \frac{R_F}{R_A} \right)}{s^2 + s^3 \frac{1}{R_C} + \left(\frac{1}{R_C} \right)^2}$

es tracta d'una reacció realimentació positiva ja que $\left[k = -\frac{1}{R_C} \left(1 + \frac{R_F}{R_A} \right) < 0 \right]$

Qüestió EP7

en lloc tancat :

$$V_{outR} = H(s) V_{outAO}$$

$$V_{outAO} = -(-\alpha V_{inR} + f_R V_{outR})$$

$$V_{outR} = -H(s) \cdot (-\alpha V_{inR} + f_R V_{outR})$$

$$V_{outR} = H(s) \alpha V_{inR} - f_R H(s) V_{outR} *$$

$$V_{outR} (1 + f_R H(s)) = H(s) \alpha V_{inR}$$

$$\frac{V_{outR}}{V_{inR}} = \frac{H(s) \alpha}{1 + f_R H(s)} = H_R(s)$$

$$H_R(s) = \frac{-\frac{R_F}{R_A} \cdot \frac{1/RC \cdot s}{s^2 + s^{\frac{3}{RC}} + (1/RC)^2}}{1 - \left(\frac{R_F}{R_A} + 1\right) \frac{1/RC \cdot s}{s^2 + s^{\frac{3}{RC}} + (1/RC)^2}} \quad \left. \begin{array}{l} H(s)\alpha \\ 1 + f_R H(s) \end{array} \right\} =$$

$$= \frac{-\frac{R_F}{R_A} \cdot \frac{1/RC \cdot s}{s^2 + s^{\frac{3}{RC}} + (1/RC)^2}}{s^2 + s^{\frac{3}{RC}} + (1/RC)^2} =$$

$$= \frac{s^3 + s^{\frac{3}{RC}} + (1/RC)^2 - \left(\frac{R_F}{R_A} + 1\right) 1/RC \cdot s}{s^2 + s^{\frac{3}{RC}} + (1/RC)^2}$$

$$= \frac{-\frac{R_F}{R_A} \cdot 1/RC \cdot s}{s^2 + s^{\frac{3}{RC}} + (\frac{1}{RC})^2 - \left(\frac{R_F}{R_A} + 1\right) \cdot 1/RC \cdot s} =$$

$$= \boxed{\frac{-\frac{R_F}{R_A} \cdot 1/RC \cdot s}{s^2 + s \left(\frac{2}{RC} - \frac{R_F}{R_A \cdot RC}\right) + (\frac{1}{RC})^2}}$$




Qüestió EP8

$$\omega_0 = \frac{1}{RC}$$

$$A = -\frac{R_F}{R_A}$$

$$\frac{2}{RC} - \frac{R_F}{RARC} = \frac{1}{RC} \cdot \frac{1}{Q}$$

$$Q = \frac{R_A}{2R_A - R_F}$$

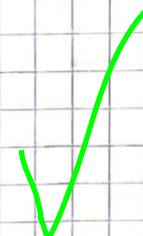

Qüestió EP9

$$Q = 5$$

$$R_A = 10k\Omega$$

$$Q = 10$$

• R_F i f_R per a $Q = 5$

$$Q = \frac{R_A}{2R_A \cdot R_F} \rightarrow 5 = \frac{10k\Omega}{2 \cdot 10k\Omega \cdot R_F}$$

$$R_F = 18k\Omega$$

$$-f_R = \frac{R_F}{R_A} + 1 \rightarrow -f_R = \frac{18k\Omega}{10k\Omega} + 1$$

$$f_R = -\frac{14}{5}$$



• R_F i f_R per a $Q = 10$

$$Q = \frac{R_A}{2R_A \cdot R_F} \rightarrow 10 = \frac{10k\Omega}{2 \cdot 10k\Omega \cdot R_F}$$

$$R_F = 10k\Omega$$

$$-f_R = \frac{R_F}{R_A} + 1 \rightarrow -f_R = \frac{10k\Omega}{10k\Omega} + 1$$

$$f_R = -\frac{29}{10}$$

Questió EPNO

$$H_{RC(s)} = \frac{-\frac{R_f}{R_A} - \frac{1}{RC} \cdot s}{s^2 + s \left(\frac{2}{RC} - \frac{R_f}{R_A R_C} \right) + \left(\frac{1}{RC} \right)^2}$$

$$s^2 + \frac{\omega_0}{Q} s + \omega_0^2 = 0 \rightarrow$$

equació en grau

$$s = \frac{-\omega_0 \pm \sqrt{(\frac{\omega_0}{Q})^2 - 4\omega_0^2}}{2} = \frac{1}{2} \left(-\frac{\omega_0}{Q} \pm \sqrt{\left(\frac{\omega_0}{Q}\right)^2 - 4\omega_0^2} \right) =$$

$$= \frac{1}{2} \left(-\frac{\omega_0}{Q} \pm \sqrt{\frac{\omega_0^2 - 4\omega_0^2 Q^2}{Q^2}} \right) = \frac{1}{2} \left(-\frac{\omega_0}{Q} \pm \sqrt{\omega_0^2 \left(\frac{1 - 4Q^2}{Q^2} \right)} \right) =$$

$$= \frac{1}{2} \left(-\frac{\omega_0}{Q} \pm \omega_0 \sqrt{\frac{1}{Q^2} - 4} \right) = \frac{1}{2} \left(-\frac{\omega_0}{Q} \pm j\omega_0 \sqrt{4 - \frac{1}{Q^2}} \right) =$$

$$= \boxed{\frac{-\omega_0}{2Q} \pm j\omega_0 \sqrt{1 - \frac{1}{(2Q)^2}}}$$



$$|H(j\omega_0)| = \frac{-\frac{R_f}{R_A} \cdot \omega_0 \cdot \omega}{\sqrt{\left(\frac{\omega_0}{2Q}\right)^2 + \left(\omega + \omega_0 \sqrt{1 - \frac{1}{(2Q)^2}}\right)^2} \cdot \left(\left(\frac{\omega_0}{2Q}\right)^2 + \left(\omega - \omega_0 \sqrt{1 - \frac{1}{(2Q)^2}}\right)^2\right)}$$

$$= \frac{-\frac{R_f}{R_A}}{\sqrt{\left(\left(\frac{1}{2Q}\right)^2 + \left(1 + \sqrt{1 - \frac{1}{(2Q)^2}}\right)^2\right) \left(\left(\frac{1}{2Q}\right)^2 + \left(1 - \sqrt{1 - \frac{1}{(2Q)^2}}\right)^2\right)}}$$

* per a $Q = 10 \rightarrow |H(j\omega_0)| = 19$

$$Q = 5 \rightarrow |H(j\omega_0)| = 9$$



Qüestió EP11

$$\omega_0 = 6250 \text{ rad/s}$$

$$Q = 10 \rightarrow s = \frac{-\omega_0}{2Q} \pm j\omega_0 \sqrt{1 - \frac{1}{(2Q)^2}} =$$

$$= \frac{-6250}{2 \cdot 10} \pm j6250 \sqrt{1 - \frac{1}{(2 \cdot 10)^2}} =$$

$$= \boxed{-312,5 \pm j6242,18}$$



$$Q = 5 \rightarrow s = \frac{-\omega_0}{2Q} \pm j\omega_0 \sqrt{1 - \frac{1}{(2Q)^2}} =$$


$$= \frac{-6250}{2 \cdot 5} \pm j6250 \sqrt{1 - \frac{1}{(2 \cdot 5)^2}} =$$

$$= \boxed{-625 \pm j6218,67}$$



$$Q = 5 \rightarrow \frac{R_F}{R_A} = 1,8$$

$$Q = 10 \rightarrow " " = 1,9$$

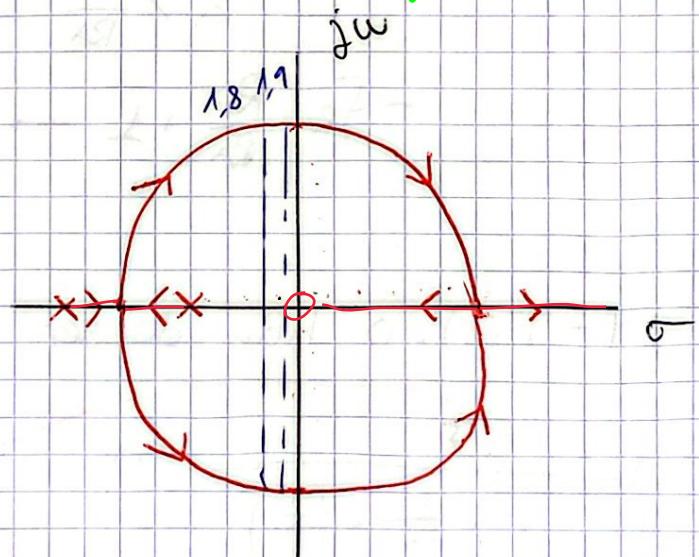

LGA acaba en
el zero a l'origen!.

Qüestió EP12

- $-\frac{\omega_0}{2Q} > 0 \rightarrow$ punt real estable

- Sabem que ω_0 es positiu de forma que $-Q > 0$; això implica que:

$$-Q = -\frac{R_A}{2R_A - R_F} = -\frac{1}{2} + \frac{R_A}{R_F}$$

$$-\frac{1}{2} + \frac{R_A}{R_F} > 0$$

$$-\frac{1}{2} > \frac{R_A}{R_F}$$

$$\frac{1}{2} < \frac{R_A}{R_F}$$

$$2 > \frac{R_F}{R_A}$$

$$-f_R = \frac{R_F}{R_A} + 1 \rightarrow -f_R < 3$$

$$f_R > -3$$



- $1 + T(s) = 0$ han de ser imaginaris (per a oscilació).

$$1 - \frac{k's}{s^2 + \frac{3}{RC} + \left(\frac{1}{RC}\right)^2} = 0 \quad k' = -k = \frac{1}{RC} \left(\frac{R_F}{R_A} + 1 \right)$$

Les nous valors positius.

$$s^2 + \frac{3}{RC}s + \frac{1}{R^2C^2} - k's = s^2 + \left(\frac{3}{RC} - k'\right)s + \frac{1}{R^2C^2} = 0$$

↳ coeficient ha de ser nul.

$$\frac{3}{RC} - k' = 0 \rightarrow 1 + \frac{R_F}{R_A} = 3 \rightarrow \boxed{\frac{R_F}{R_A} = 2} \quad \begin{matrix} \text{condició} \\ \text{de oscilació} \end{matrix}$$

$$R_F = 2R_A = 2 \cdot 10k\Omega = \boxed{20k\Omega}$$

