

# Estudi previ practica 6 sessió 2

## exercici 2.1

$$\frac{1}{f_{osc}} = (R_{s1} + 2R_{s2}) \cdot C_{s1} \cdot \ln(2)$$

$$R_{s2} = 54,15 \text{ k}\Omega$$

$$\frac{T_H}{T} = \frac{(R_{s1} + R_{s2}) \cdot C_{s1} \cdot \ln(2)}{(R_{s1} + 2R_{s2}) \cdot C_{s1} \cdot \ln(2)} = 0,5$$

## exercici 2.2

• ~~Mantindre la estabilitat a la sortida~~

*Netejar les interferències que apareixen en la tensió d'aquest node*

## exercici 2.3

$$T_{of} = \frac{2 \cdot d}{V} = \frac{2 \cdot 6}{340} = 0,0353$$

$$f_{REP} = \frac{1}{0,0353} = 28,3 \text{ Hz}$$

## exercici 2.4

$$T = \frac{N_{cicles}}{f_{osc}} = \frac{10}{40k} = 250 \mu s$$

## exercici 2.5

$$T = 250 \cdot 10^{-6} = \ln\left(\frac{2V_{cc} - 2,1}{V_{cc} - 2,1}\right) \cdot R_{61} \cdot C_{61}$$

$$R_{61} = \frac{250 \cdot 10^{-6}}{\ln\left(\frac{24 - 2,1}{12 - 2,1}\right) \cdot 220 \cdot 10^{-9}} = 1431,28 \Omega$$

## exercici 2.6

$$\frac{1}{f_{REP}} = (R_{61} + R_{62}) \cdot C_{61} \cdot \ln(2)$$

$$f_{REP} = \frac{1}{(221431,28) \cdot 220 \cdot 10^{-9} \cdot \ln(2)} = 29,62 \text{ Hz}$$